

USN

--	--	--	--	--	--	--	--	--	--

10CS33

Third Semester B.E. Degree Examination, Dec.2015/Jan.2016
Logic Design

Time: 3 hrs.

Max. Marks:100

Note: Answer any FIVE full questions, selecting atleast TWO questions from each part.

PART - A

- 1 a. What is Logic gate? State and prove De Morgan's theorems. (07 Marks)
b. Describe positive and negative logic. Prove "positive OR" logic equal to "Negative AND" logic. (05 Marks)
c. Implement the following function by using : i) Nand gates only ii) NOR gates only.
 $Y = ((A + B).C) . D$ (08 Marks)
- 2 a. Find the minimal SOP and minimal POS of the following Boolean function using K - Map.
 $f(a, b, c, d) = \Sigma_m(6, 7, 9, 10, 13) + d(1, 4, 5, 11)$. (08 Marks)
b. Using Q.M method simplify the following expression and realize it by using Nand logic only. $f(a, b, c, d) = \Sigma(0, 3, 5, 6, 7, 11, 14)$. (10 Marks)
c. Write a note on Static Hazard. (02 Marks)
- 3 a. Construct 8:1 multiplexer using only 2:1 multiplexer. (06 Marks)
b. Mention the three differences between decoder and demultiplexer. (03 Marks)
c. Write the four comparisons between PLA and PAL. (04 Marks)
d. Implement the following function using PLA : (07 Marks)
 $A(x, y, z) = \Sigma_m(1, 2, 4, 6)$; $B(x, y, z) = \Sigma_m(0, 1, 6, 7)$: $C(x, y, z) = \Sigma_m(2, 6)$.
- 4 a. With logic diagram and truth table, explain the working of master slave (J, K) flip flop. (06 Marks)
b. Draw the logic truth table and timing diagram of positive edge triggered D – flip flop. (06 Marks)
c. Write the verilog code for positive edge triggered J.K flip flop. (03 Marks)
d. With neat diagram, explain the working principles of Switch De bouncer circuit. (05 Marks)

PART - B

- 5 a. Write a note on classifications of Registers. (04 Marks)
b. With neat diagram and timing diagram, explain the working of Serial in – Serial out register. For explanation construct 4 bit register using J.K flip flops. (10 Marks)
c. Write a Verilog code for : i) Switched tail counter ii) Shift registers of 5 bits constructed using D-flip flops. (06 Marks)
- 6 a. Write the comparison between Synchronous and Asynchronous counter. (04 Marks)
b. Design : i) a divide by 78 counter using 7493 and 7492 IC ii) modulo 120 counter using 7490 and 7492 IC. (08 Marks)
c. Design a mod 6 counter using J.K flip flops and K – map simplification method. (08 Marks)
- 7 a. Explain the difference between Mealy model and Moore model. (05 Marks)
b. Design a Mealy type sequence detector to detect a serial i/p sequence of 101. (10 Marks)
c. How does state transition diagram of a Moore machine differ from Melay machine? (05 Marks)
- 8 a. Explain with neat diagram, successive approximation A/D converter. (06 Marks)
b. Explain with neat diagram, counter method of A/D conversion. (06 Marks)
c. Write short notes on :
i) Binary loader ii) Differences between D/A and A/D converters. (08 Marks)
