

(3 Hours)

[Total Marks: 80]

N.B.: (1) Question No. 1 is compulsory.

(2) Solve any **three** questions out of remaining **five**.(3) Figures to **right** indicate **full** marks.(4) Assume suitable **data** where **necessary**.

- Q1. Solve any four 20
- State ideal and Practical Characteristics of an Op-amp
  - Explain Multiplexer and Demultiplexer.
  - Convert following decimal number to Binary ,Octal, Hexadecimal and Gray code
    - $(128)_{10}$
    - $(73)_{10}$
  - Explain working of LCD.
  - Covert D flip flop to S-R flip flop.
- Q2. a) a) Implement following using only one 8:1 Multiplexer and few gates. 10
- $$F(A,B,C,D) = \sum m(0,1,3,4,5,8,9,10,12,15)$$
- b) Explain Fixed Biasing Circuit with its stability factor. 10
- Q3. a) Draw and Explain Instrumentation Amplifier using Op-amp. 10
- b) Draw circuit diagram and explain the operation of Monostable Multivibrator using IC555. 10
- Q4. a) Minimize the following four variable logic function using K-map and design 10
- by using basic gates
- $$f(A,B,C,D) = \sum m(0,1,2,3,4,7,8,9,11,15)$$
- b) What are the different methods used to improve CMRR in Differential Amplifier. 10
- Explain one in brief. 10
- Q5. a) Design a Mod 12 asynchronous counter using J-K-flip flop 10
- b) Design 4-bit binary to gray code conversion 10
- Q6 Write short notes on any four 20
- Explain the working of a Non-inverting amplifier using Op-amp
  - Explain working of a transistor.
  - Write VHDL program for NAND gate.
  - Explain working of Current Mirror Circuit.
  - Explain block diagram of op-amp.

\*\*\*\*\*