

Sub : Linear Integrated circuits & Design  
TE (ETRX) V (Rev)  
21/5/2014  
QP Code : MV-18440

(3 Hours)

[Total Marks : 100

- N.B. :** (1) Question No. 1 is compulsory.  
(2) Answer any **four** out of the remaining **six** questions.  
(3) Assume **suitable** data wherever **necessary**.  
(4) Figures to **right** indicate **full** marks.

1. Solve any **four** :—

20

- Explain CMRR measurement procedure with examples.
- How is current boosting achieved in a 723 IC ?
- What are the different linear IC packages ?
- What is rolloff rate of first order filter ?
- Draw sample and hold Amplifier and list its applications.
- Explain first order Active filter circuit.

2. (a) Draw simplified Op-Amp circuit diagram and explain the following stages alongwith the working of this circuit :— 10

- Input Stage
- Second Stage
- Output Stage.

(b) Draw the circuit diagram of three Op-Amp instrumentation amplifier. Get an expression for the output. State its characteristics. 10

3. (a) Design a fourth order Butterworth Low pass filter having upper cut-off frequency of 1kHz. 10

(b) What is a Switched Capacitor ? Give the circuit of a Switched Capacitor Low pass filter and discuss various types of Switched Capacitor ? 10

4. (a) What are the different types of Digital to analog Converters ? Explain one of the techniques in detail. 10

(b) What is Comparator ? Draw the characteristics of an ideal Comparator and that of a commercially available Comparator. What is the difference between a basic Comparator and the schmitt trigger ? 10

[ TURN OVER

5. (a) Draw and explain the functional diagram of Timer IC 555 and explain its operation in astable mode. 10
- (b) Draw and explain the circuit diagram to generate square and triangular waveforms using Op-Amp. Derive the expression for frequency and Comment about the range of frequency. 10
6. (a) What is the function of voltage regulator ? Explain in detail about fixed voltage series regulator. 10
- (b) Design a voltage regulator using IC 723 for  $V_o = 5V$ ,  $I_o = 50 \text{ mA}$ ,  $I_{SC} = 75 \text{ mA}$ ,  $V_{in} = 15 \text{ V}$ . Assume  $V_{sense} = 0.6 \text{ V}$ . 10
7. Write short notes on any four of the following :— 20
- (a) RC phase shift oscillator
  - (b) KRC filter
  - (c) Peak detector
  - (d) Phase Locked Loop
  - (e) Voltage to frequency converters.
-