

Total No. of Questions—8]

[Total No. of Printed Pages—3

Seat No.	
-------------	--

[4957]-1046

**S.E. (Electronics/Electronics and Telecommunication)**

**(II Semester) EXAMINATION, 2016**

**INTEGRATED CIRCUITS**

**(2012 PATTERN)**

**Time : Two Hours**

**Maximum Marks : 50**

- N.B. :-** (i) Answer Q. No. 1 or Q. No. 2, Q. No. 3 or Q. No. 4,  
Q. No. 5 or Q. No. 6, Q. No. 7 or Q. No. 8,  
(ii) Neat diagrams must be drawn wherever necessary.  
(iii) Figures to the right indicate full marks.  
(iv) Use of electronic pocket calculator is allowed.  
(v) Assume suitable data, if necessary.

1. (a) What are the different types of noise those are associated with opamps ? Draw opamp noise model and give expression for output noise voltage. [6]  
(b) With neat diagram explain the necessity and working of current mirror circuit. [6]

*Or*

2. (a) Following specifications are given for dual input balance output difference amplifier : [6]

P.T.O.

$R_C = 2.2 \text{ K}\Omega$ ,  $R_E = 4.7 \text{ K}\Omega$ ,  $R_{in1} = R_{in2} = 50 \text{ }\Omega$ ,  $+V_{CC} = 10 \text{ V}$ ,  $-V_{EE} = -10 \text{ V}$ ,  $\beta_{ac} = \beta_{dc} = 100$ ,  $V_{BE} = 0.715 \text{ V}$ .

Determine :

- (i) Operating point i.e.  $I_{CQ}$  and  $V_{CEQ}$
  - (ii) Input and output resistance.
- (b) What is the need of frequency compensation ? Explain any one method of external frequency compensation. [6]
3. (a) Explain practical differentiator circuit with neat circuit diagram. What are the limitations of ideal differentiator ? [6]
- (b) Draw and explain sample and hold circuit using Op-amp. [6]
- Or*
4. (a) Draw and explain half wave precision rectifier circuit. [6]
- (b) Explain the working of inverting Schmitt trigger. Also derive the equations for the trigger points. [6]
5. (a) Explain V2F converter with appropriate waveforms. [7]
- (b) Explain binary weighted resistor type of DAC. [6]

*Or*

6. (a) With the help of neat diagram explain the operation of Dual Slope ADC. [7]
- (b) Calculate output voltage of 8 bit DAC for digital input 10000000 and 11011101 with reference voltage of 10 V. [6]

7. (a) With the help of neat block diagram explain operation of PLL.  
Define the terms Lock range and Capture range. [7]
- (b) Write a short note on fixed and variable voltage regulators. [6]

*Or*

8. (a) Draw and explain circuit of FM demodulator using PLL. [7]
- (b) Explain low drop out voltage regulator. [6]

stupidstid.com