

Note: 1) Question no. 1 is compulsory.

2) Solve any three questions out of remaining.


3) Fig. to the right indicates maximum marks.

4) Assume suitable data wherever necessary but justify the same.

Q1. Solve any five.

(5x4 = 20)

 a) Determine the value of  $R_c$  such that  $V_c = 5V$  and  $\beta = 50$ .




b) State and explain Miller's Theorem.

c) Design a self bias circuit using JFET for  $I_D = 3mA$ ,  $V_{DD} = 20V$  and  $V_{DS} = 0.6 V_{DD}$ .  
(  $I_{DSS} = 8mA$ ,  $V_P = -4V$  )

d) Explain various types of capacitors.

 e) Determine the values of coupling capacitors  $C_{C1}$  and  $C_{C2}$  if  $r_{\pi} = 1.5K\Omega$ ,  $\beta = 120$  and  $f_L = 20Hz$ .




f) Explain concept of zero temperature drift in JFET.

[TURN OVER

Q2. A) Calculate 1)  $I_{BQ}$ ,  $I_{CQ}$  2)  $g_m$ ,  $r_{\pi}$  3) Small signal voltage gain 10


For the circuit given below.

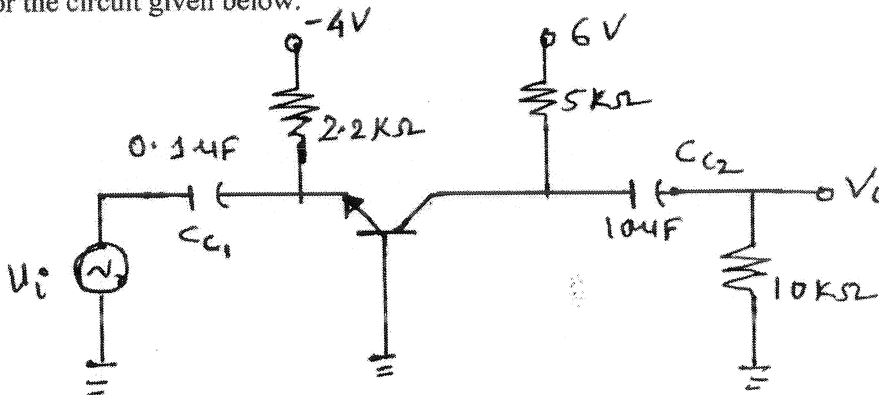

Q2 B) Explain the concept of LC filter in power supply circuit and hence derive expression for ripple factor of LC filter. 10

Q3 A) Explain concept of shunt Zener regulator. For a shunt Zener regulator giving output voltage of 10 V and load resistance varying from  $5K\Omega$  to  $10K\Omega$ ,  $V_{in}$  is varying between 18V to 22V. Find  $R_s$ ,  $P_{zmax}$ ,  $S_v$  and  $R_o$ . Assume  $R_z = 4\Omega$  and  $I_{zmin} = 50\mu A$ . 10

 B) Determine  $I_{DQ}$ ,  $V_{GSQ}$ ,  $V_{DSQ}$  if  $I_{DSS} = 9mA$  and  $V_p = -3V$  for the circuit given below. 10



Q4 A) Design capacitive filter with FWR using two diodes with ripple factor less than 5%. 10  
Output voltage is 24V and load current 200mA. The input line voltage of 230V/ 50Hz is available.

B) Determine the values of biasing components for a CE configuration if  $V_{CC} = 12V$ ,  $V_{CE} = 6V$ ,  $R_C = 1K\Omega$ ,  $V_{BE} = 0.6V$ ,  $\beta = 180$  for the following circuit. 10  
i) Fixed bias without  $R_E$   
ii) Voltage Divider bias with  $V_{RE} = 10\%$  of  $V_{CC}$  and  $S_1 = 8$

[TURN OVER


Q5 A) For JFET if  $I_{DSS} = 6 \text{ mA}$ ,  $V_P = -6\text{V}$   $r_d = \infty$ ,  $C_{gd} = 4\text{pF}$ ,  $C_{gs} = 6\text{pF}$ ,  $C_{ds} = 1\text{pF}$  15

Determine i)  $V_{GSQ}$  ii)  $I_{DQ}$

iii)  $g_{mo}$  iv)  $g_m$

v) Midband voltage gain  $A_v$

vi) Higher cut off frequency

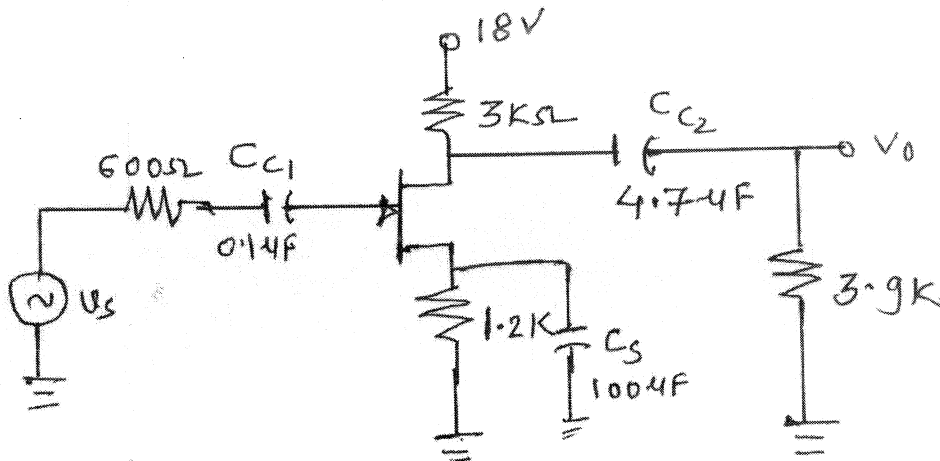

B) Explain high frequency  $\Pi$  equivalent model of common emitter BJT.

5

Q6. Design single stage CS amplifier using mid-point biasing method for voltage gain of 12, 20

$F_L = 20 \text{ Hz}$ ,  $R_L = 10\text{k}\Omega$ ,  $V_o = 3.5\text{V}$

(Use JFET parameters  $I_{DSS} = 7\text{mA}$ ,  $V_P = -2.5\text{V}$ ,  $g_{mo} = 5600\mu\text{S}$ ,  $r_d = 50\text{k}\Omega$ )