


Time: 3 hours

Total Marks: 80


N.B.

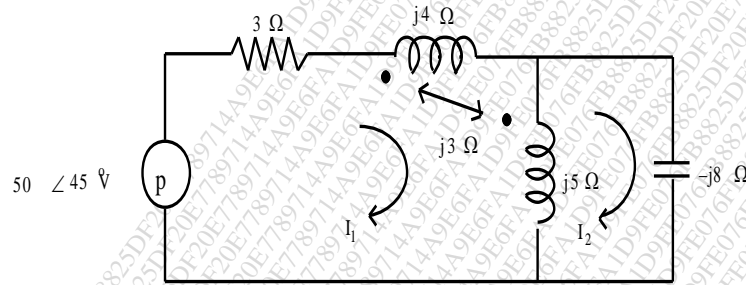- 1) Question No. 1 is Compulsory
- 2) Out of remaining questions, attempt any three
- 3) Assume suitable data if required
- 4) Figures to the right indicate full marks

- 1 (A) Draw equivalent circuit for given magnetically coupled circuit. 05




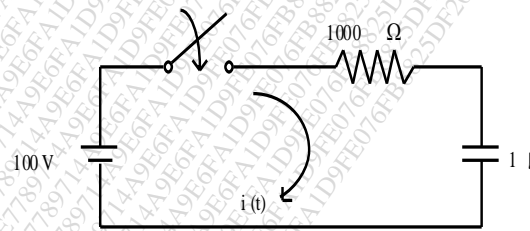- (B) In the network of Fig. switch is closed at  $t = 0$ . With capacitor uncharged, find value for  $i$  and  $\frac{di}{dt}$  at  $t = 0^+$ . 05




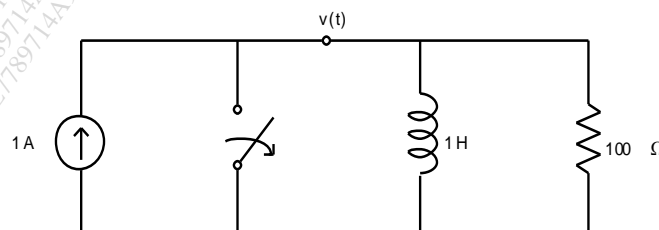- (C) Prove that  $AD - BC = 1$  for Transmission parameters. 05
- (D) Design an  $m$ -derived T section high pass filter with a cut-off frequency of 2 kHz. Design impedance of  $700\Omega$  and  $m = 0.6$ . 05


- 2 (A) In the network shown in Fig., at  $t = 0$ , switch is opened. Calculate  $v$ ,  $\frac{dv}{dt}$ ,  $\frac{d^2v}{dt^2}$  at  $t = 0^+$ . 10



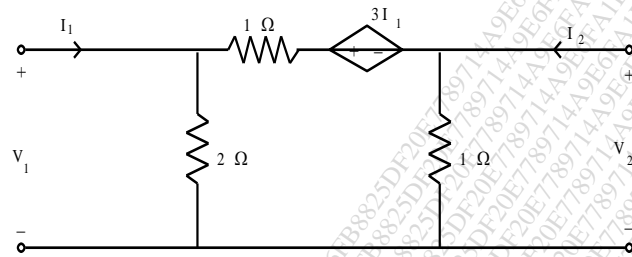(B) For the network shown in Fig., find Y and Z-parameters. 10



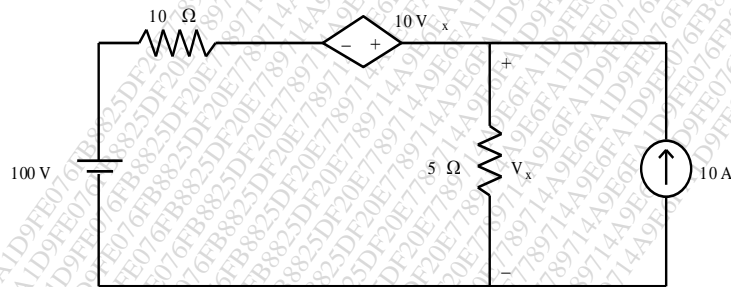3 (A) Determine the current through 10 Ω resistor in the network of Fig. 10




(B) The parameters of a transmission lines are  $R = 65\Omega/\text{km}$ ,  $L=1.6\text{mH}/\text{km}$ ,  $G = 2.25$  10  
 $\text{mmho}/\text{km}$ ,  $C=0.1\mu\text{F}/\text{km}$ . Find  
 i) Characteristic Impedance  
 ii) Propagation Constant  
 iii) Attenuation Constant  
 iv) Phase Constant at 1 kHz


4 (A) Determine whether following functions are positive real 10

- i)  $\frac{s^2 + 2s + 4}{(s + 1)(s + 3)}$
- ii)  $\frac{s^2 + 25s + 25}{s + 4}$

(B) Find Norton's equivalent network. 10

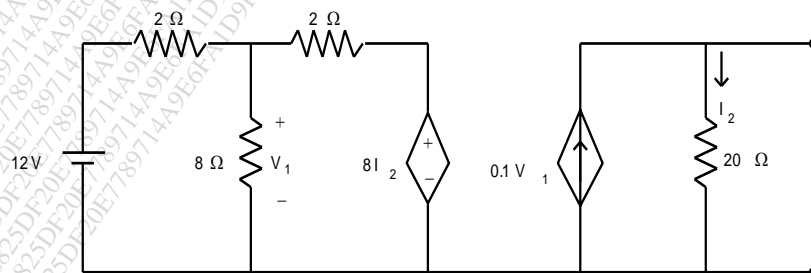

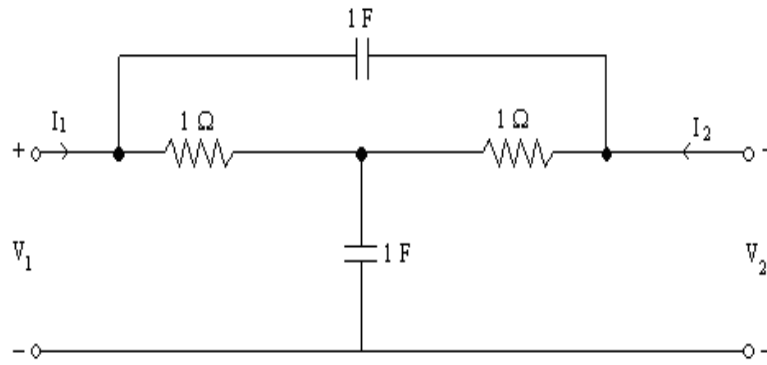- 5 (A) Find Y-parameters for the network shown in Fig. 10




- (B) Realize the following functions in Foster II and Cauer I form 10

$$Z(s) = \frac{2(s^2 + 1)(s^2 + 9)}{s(s^2 + 4)}$$

- 6 (A) A transmission line has a characteristics impedance of 50 ohm and terminate in a load  $Z_L = 25 + j50$  ohm. Use smith chart and Find VSWR and Reflection coefficient at the load. 10

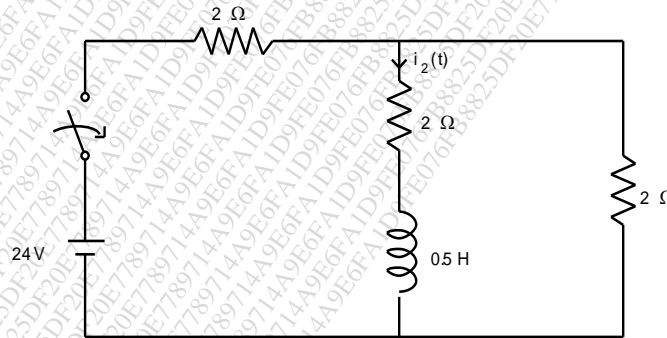- (B) Determine current  $i_2(t)$  in the network of Fig., when switch is closed at  $t = 0$ . The inductor is initially deenergized. 10



\*\*\*\*\*