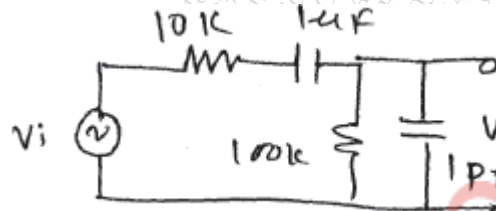


Please check whether you have got the right question paper

- N.B :**
1. Question No.1 is **compulsory**.
 2. Attempt **any three** questions from remaining.
 3. **All** questions carry **equal** marks.
 4. Assume suitable data wherever necessary.

1. Attempt **any four** of the following

- (a) Draw general frequency response of an amplifier. Determine corner frequencies for the following. 5




- (b) Compare MOSFET diffamp with passive load and active load. 5
- (c) Calculate max power dissipation with and without heat sink. 5

$$\theta_{c} = 1.5^{\circ}\text{C/W}, \theta_{CS} = 1^{\circ}\text{C/W}, \theta_{CA} = 50^{\circ}\text{C/W}$$


$$\theta_{JA} = 4^{\circ}\text{C/W}, T_{jmax} = 100^{\circ}\text{C}, T_{Amb} = 25^{\circ}\text{C}$$

- (d) State and explain Barkhausen criteria. 5
- (e) Explain working of SCR. Define I_L and I_H . 5

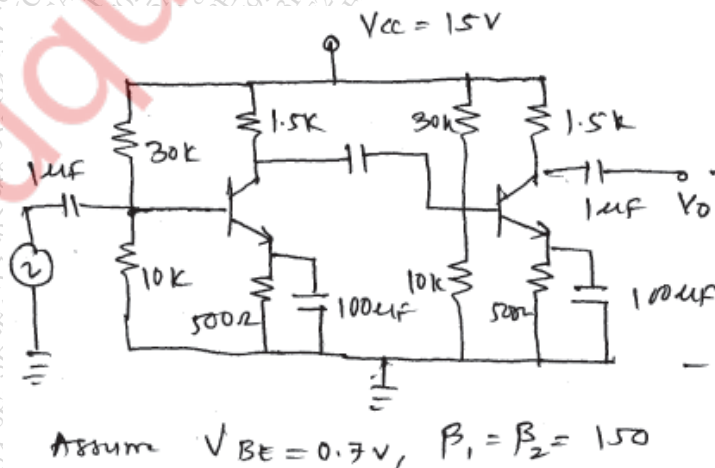2. (a) Determine voltage gain, i/p and o/p impedance for the two stage amplifier shown below. 10



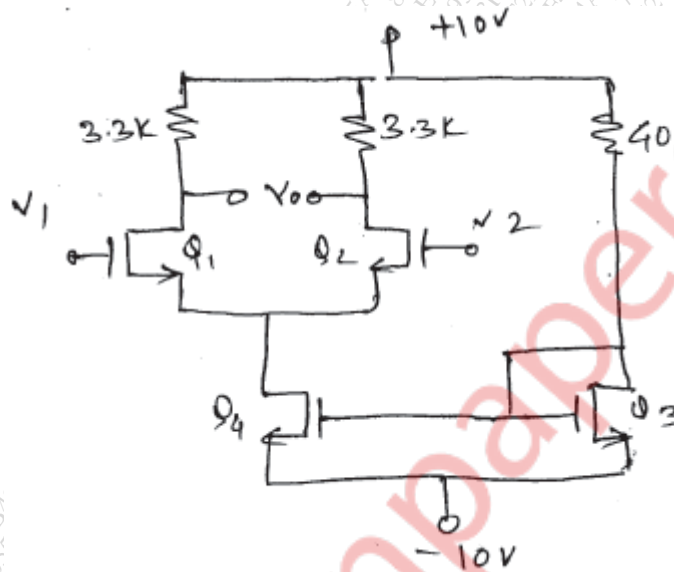- (b) Explain working of RC phase shift oscillator. Give expression for frequency of oscillations. **10**
3. (a) Draw block diagram of voltage series negative feedback. Derive formulae for A_{vf} , R_{if} , R_{of} . **10**
- (b) Explain working of UJT with the help of characteristics. Hence explain relaxation oscillator. **10**
4. (a) Determine I_{DQ} , V_{GSQ} and differential mode gain for following circuit. Assume $K_n = 0.15 \text{ mA/V}^2$, $(VA) = 100 \text{ V}$, $V_T = 1.5 \text{ V}$. **10**



- (b) Draw circuit diagram of class A Transformer coupled amplifier. Explain working, Draw AC/DC load line. Derive expression of efficiency. **10**
5. (a) Explain high frequency response of CS-MOSFET amplifier with proper equation. Discuss effects of parasitic capacitances. **10**
- (b) Explain use of constant current source in Diff amps. Give description of any one type. **10**
6. Solve (Any Three) **20**
- (1) Cascode Amplifier working
 - (2) Gunn diode and its applications
 - (3) Crossover distortion and methods to remove in class B amplifier
 - (4) Hartley oscillator.