

[Time: Three Hours]


[Marks:80]

Please check whether you have got the right question paper.

- N.B:
1. Question no. 1 is compulsory.
 2. Solve any three questions from the remaining.
 3. Assume suitable data wherever necessary.

Q.1 Attempt any four. (20)

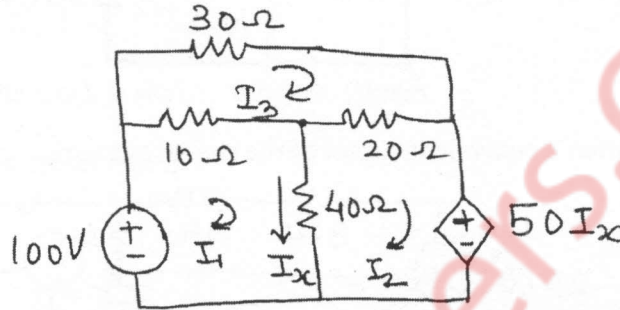(a) Find current through $20\ \Omega$ branch.



(b) Discuss the initial and steady state conditions in relationship with voltage and current for the following circuit elements.


- i) Resistor
- ii) Inductor
- iii) Capacitor

(c) Draw the oriented graph of a network with f-cutset matrix as shown:


	Twigs					links	
	1	2	3	4	5	6	7
1	1	0	0	0	-1	0	0
2	0	1	0	0	1	0	1
3	0	0	1	0	0	1	1
4	0	0	0	1	0	1	0

(d) Write the properties of positive real function.

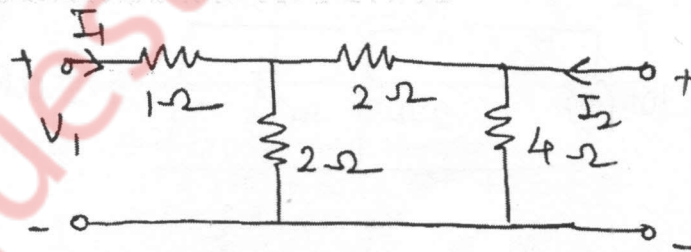
(e) Find Y-parameter for the shown network.



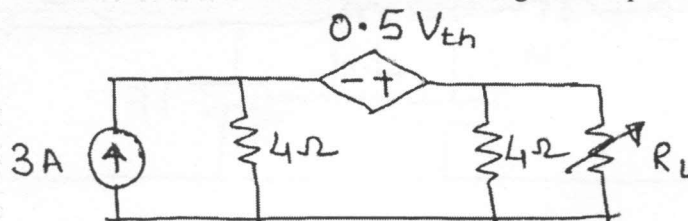
Q.2 (a) In the given network; what will be the value of R_L to get max. power delivered to it. (10)



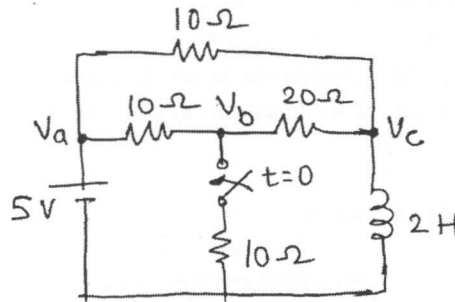- (b) In the network shown; a steady state is reached with switch open. At $t=0$ the switch is closed. For the element values given; determine the $V_a(0^-)$, $V_b(0^-)$ and $V_a(0^+)$ and $V_b(0^+)$ (10)



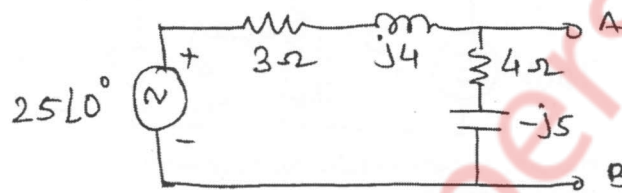
- Q.3 (a) Obtain Norton's equivalent circuit of the shown network. (05)




- (b) Obtain thevenin's equivalent source. (05)



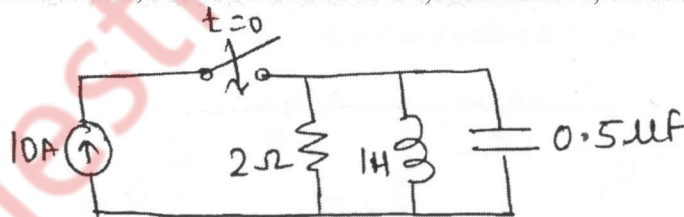
- (c) For the shown network, switch is closed at $t=0$, determine V , dv/dt and d^2v/dt^2 at $t=0^+$ (10)



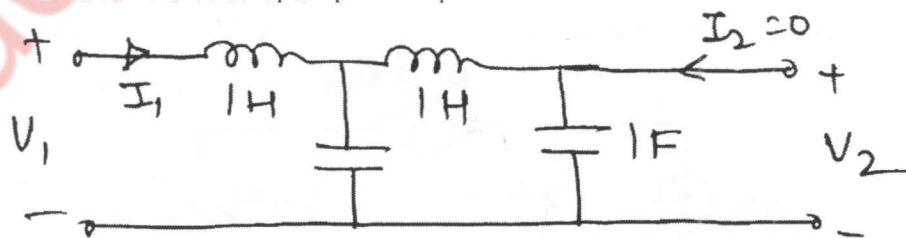
- Q.4 (a) Find network functions $\frac{V_1}{I_1}$, $\frac{V_2}{I_1}$ and $\frac{V_2}{V_1}$ for the shown network (10)



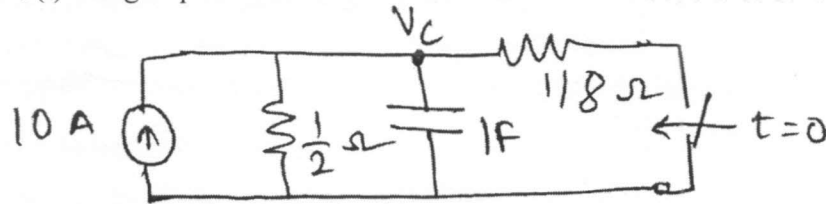
- (b) Find $V_c(t)$ using Laplace transform. If the switch is closed at $t = 0$. (10)



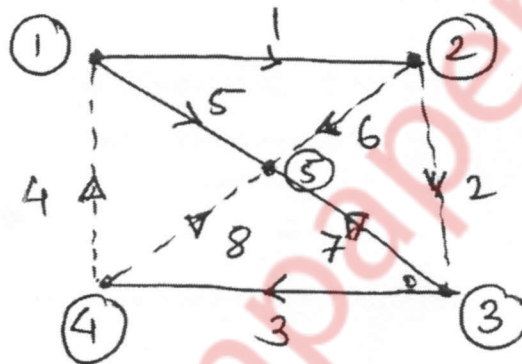- Q.5 (a) Linear graph of a network is shown in figure. Obtain (10)
 i) Incidence matrix
 ii) Fundamental cutset matrix
 iii) Fundamental tieset matrix.



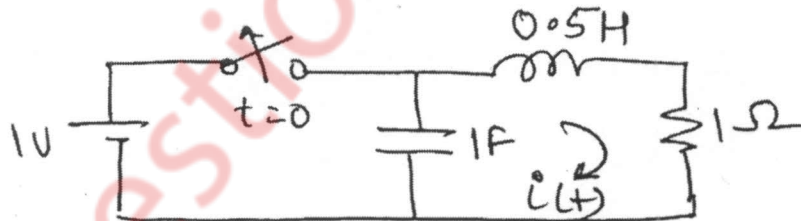- (b) In the network shown. Switch is opened at $t = 0$. Steady state condition is achieved before $t = 0$ find $i(t)$. (10)



- Q.6 (a) Check whether the following polynomials Hurwitz's or not. (10)
 i) $P(s) = 2s^6 + s^5 + 135s^4 + 6s^3 + 56s^2 + 25s + 25$
 ii) $P(s) = s^4 + 7s^3 + 6s^2 + 21s + 8$

- (b) Realize the Foster forms of the impedance function (10)

$$Z(s) = \frac{4(s^2+1)(s^2+9)}{s(s^2+4)}$$
